

Con. 7485-13.

(REVISED COURSE)

GS-3013

(3 Hours)

[Total Marks : 100]

N.B. : (1) Question No. 1 is compulsory.

(2) Attempt any **four** questions from remaining **six** questions.(3) Use Smith chart if **necessary**.(4) **Figures** to the **right** indicate **full** marks.

1. (a) Explain Large signal characterization with reference to load pull counters, how it is measured ? 5
- (b) What are the causes of low frequency noise and high frequency noise associated with the mixer ? 5
- (c) Define and explain with neat diagram noise correlation matrix for general noisy two port network. 5
- (d) What is an unilateral figure of merit of an amplifier ? 5

2. (a) If the transistor has following S-parameters at 5GHz with 50 Ω impedance. 10

$$S_{11} = 0.6 \angle -175^\circ \quad ; \quad S_{12} = 0.02 \angle 20^\circ$$

$$S_{21} = 2.2 \angle 35^\circ \quad ; \quad S_{22} = 0.6 \angle -95^\circ$$

Determine the stability criteria and plot the stability circles.

- (b) Derive following parameters of an amplifier— 10
 - (i) power gain (G)
 - (ii) Available gain (GA)
 - (iii) Transducer gain (GT).
3. (a) Explain using suitable diagrams two methods of designing broad band amplifier. 10
- (b) A BJT with $I_c = 30$ mA and $V_{CE} = 10$ V is operated at a frequency of 1.0 GHz in a 50 Ω system. Its S-parameters are— 10

$$S_{11} = 0.73 \angle 175^\circ \quad ; \quad S_{22} = 0.21 \angle -80^\circ$$

$$S_{12} = 0.0 \quad ; \quad S_{21} = 4.45 \angle 65^\circ$$

Determine whether the transistor is unconditionally stable. If yes, calculate the optimum terminations, $G_{S,max}$, $G_{L,max}$, $G_{TU,max}$.

4. (a) A certain GaAs MESFET has following noise figure parameters measured at 15 V_{ds} = 50, I_{ds} = 20 mA with 50 Ω resist once for frequency of 9 GHz, 15

$$F_{min} = 4\text{dB}, \Gamma_{opt} = 0.55 \angle 175^\circ, R_0 = 4 \Omega$$

Plot noise figure circles for given values of f_1 at 2, 2.5, 3.5, 4.5 dB.

- (b) Define stability. List the various criteria for stability. 5

[TURN OVER

Con. 7485-GS-3013-13.

2

5. (a) If a one port microwave diode has $\Gamma_{in} = 1.5 \angle 60^\circ$ with respect to $Z_0 = 50 \Omega$. 12

Design an oscillator for desired frequency of 10 GHz.

- (b) For two port oscillator at steady-state oscillation prove that if :— 8

$$\Gamma_L \Gamma_{in} = 1 \text{ then } \Gamma_{in} \Gamma_{out} = 1$$

6. A certain MESFET is biased for large signal class A operation with the following 20
small signal S-parameters at 5 GHz :—

$$S_{11} = 0.55 \angle -150^\circ ; S_{12} = 0.04 \angle 20^\circ \quad S_{21} = 3.5 \angle 170^\circ \quad S_{22} = 0.45 \angle -30^\circ ;$$

The large signal forward transmission coefficient S_{21} is measured to be $S_{21} = 2.8 \angle 180^\circ$. Design a Large – Signal Class A amplifier with maximum transducer gain in a 50Ω system. Assume ± 0.5 dB error in gain. What is the high-power amplifier gain ?

7. (a) Write a note on optimal loading used in 1 + PA design. 10
(b) A wideband amplifier (2 – 4 GHz) has gain of 10dB, an O/P power of 10 dBm 10
and a noise figure of 4 dB at room temperature. Find the output noise power in dBm.
